

Digital Logic Design – Lab #1


Any logic gate can be constructed from only NAND gates. To construct an XOR gate I first made two truth tables, one for a NAND gate and one for an XOR gate. I then did the Boolean algebra and took a simplified expression for an XOR gate and turned it into one which uses NAND's.

NAND Gate

Input 1	Input 2	Output
0	0	1
0	1	1
1	0	1
1	1	0

XOR Gate

Input 1	Input 2	Output
0	0	0
0	1	1
1	0	1
1	1	0

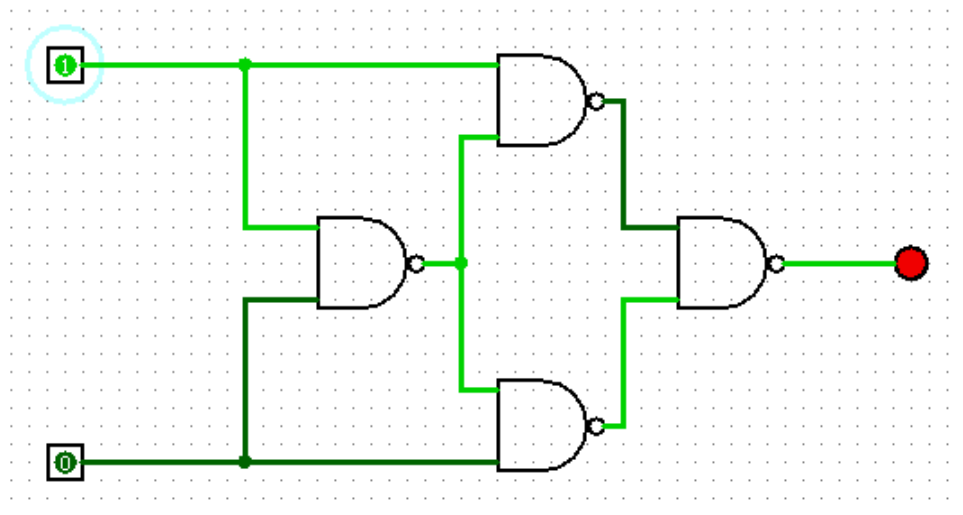

Boolean algebra:

$$A'B + AB'$$

(Simplified XOR Gate)

$$AA' + A'B + AB' + BB'$$

$$A(A+B)' + B(A+B)'$$

$$A(A'B') + B(A'B')$$

$$A'(A'B') + B'(A'B')$$

$$(A(A'B'))'(B(A'B'))'$$

(XOR Gate with NAND gates)